

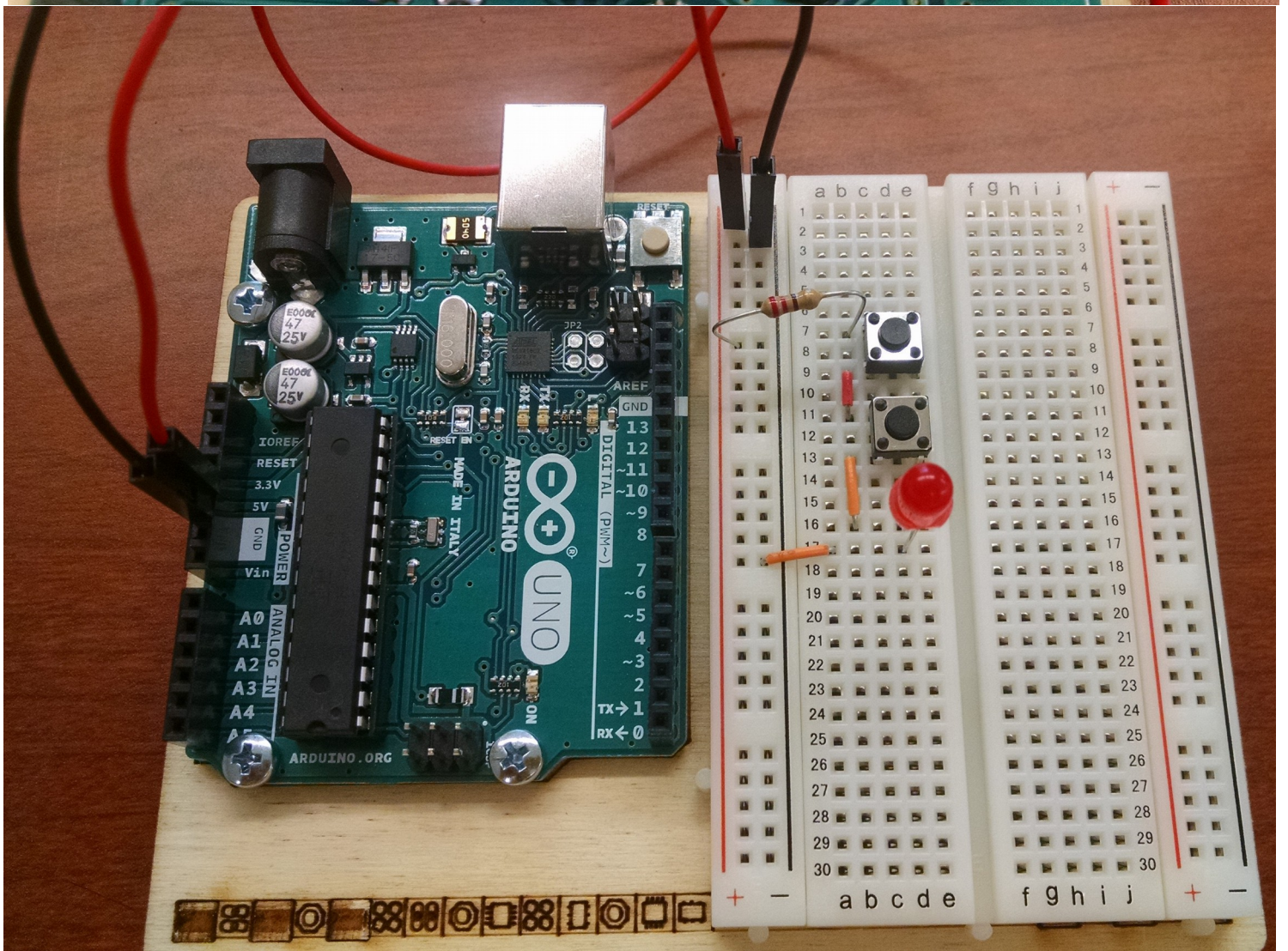


Project 1: series circuit

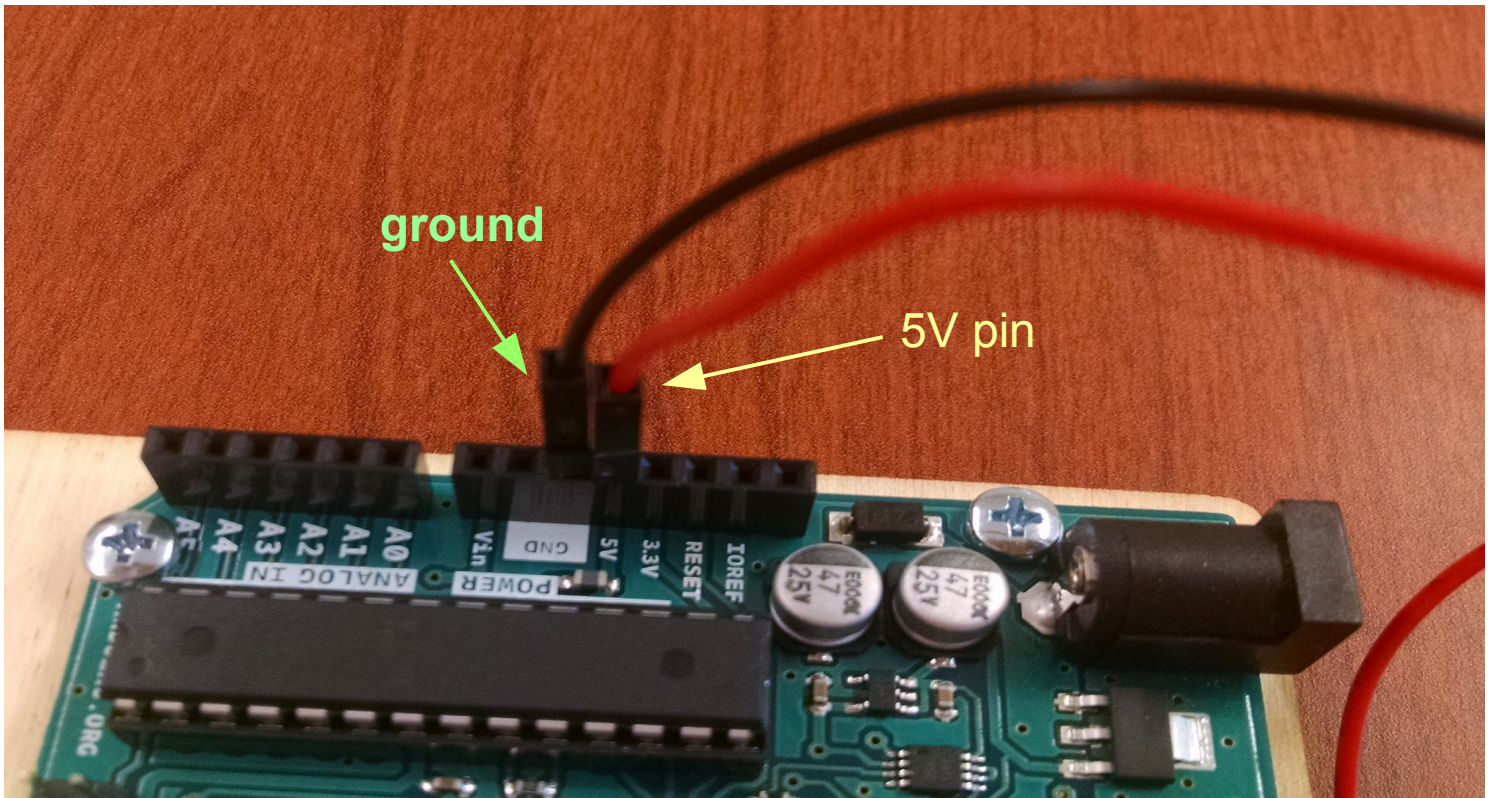

Project 1b: Parallel circuit

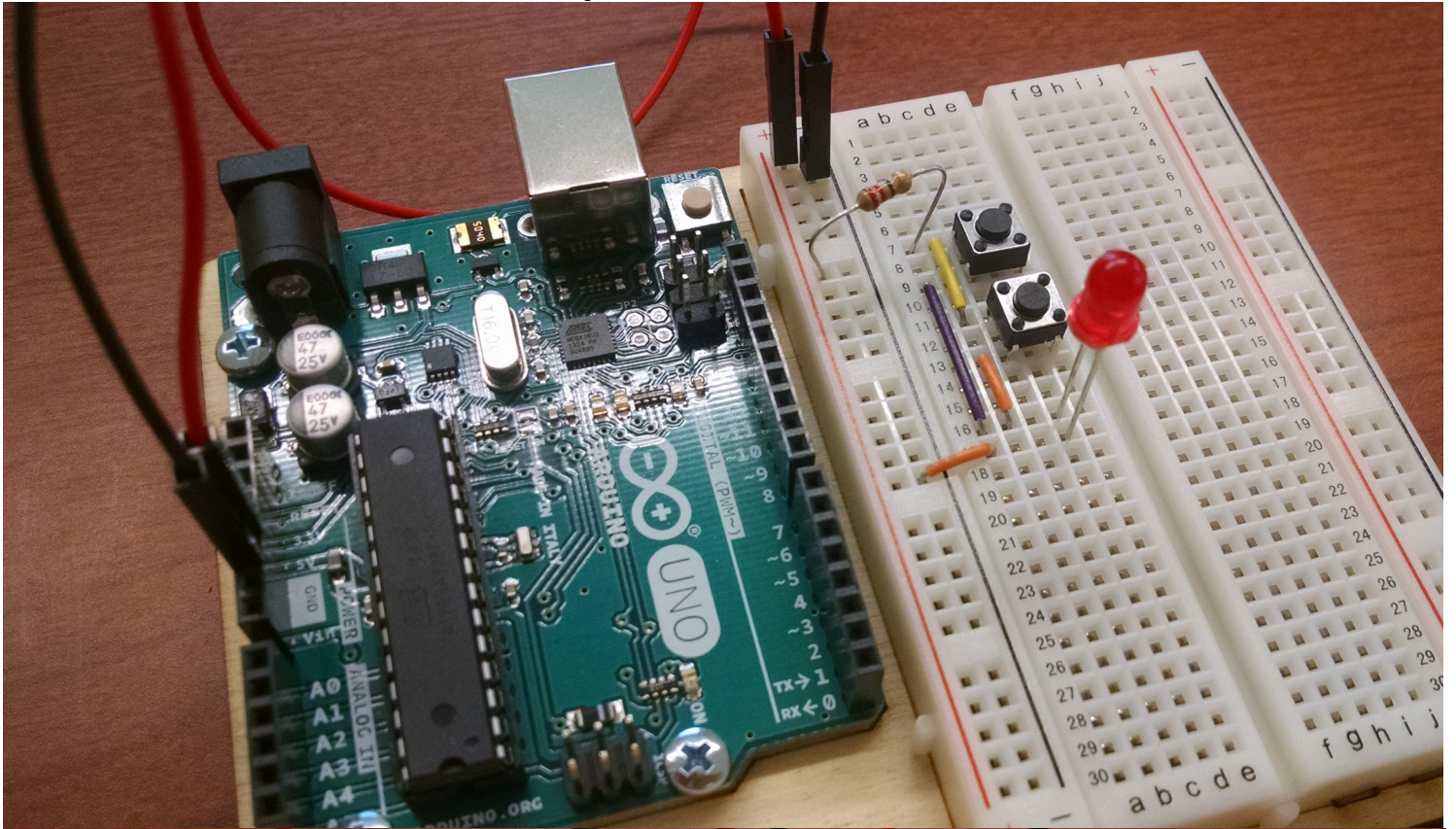

Project 2: Spaceship interface → Traffic Light???

